

Name: MAHFUZA KHATUN

ID : 2112376111

Course code: CSE-1212

Course Title: Introduction to Digital.  
Electronics Lab

Session : 2020-21

Department name: Computer Science and  
Engineering

## Design And Implementation of Code Converter :

### Aim:

To design and implement 4-bit

- i) Binary to Gray Code Converter
- ii) Gray to Binary Code Converter
- iii) Binary to Excess-3 Code Converter
- iv) Excess-3 to binary code converter

### Theory

The availability of large variety of codes for the discrete elements of information results in the use of different codes by different systems. A conversion circuit must be inserted between the two systems if each uses different codes for same information. Thus, Code Converter is a circuit that makes the two systems compatible even though each uses different binary code.

The bit combination assigned to binary code to gray code. Since each code uses four bits to represent a decimal digit. There are four inputs and four outputs. Gray code is a non-weighted code. The input variables are designed as  $B_3, B_2, B_1, B_0$  and the output variables are designated as  $G_3, G_2, G_1, G_0$  from the truth table, combinational circuit is designed. The boolean functions are obtained from K-map for each output variable.

A Code Converter is a circuit that makes the two systems compatible even though each uses a different binary code. To convert from binary to excess-3 code, the input line must supply the bit combination of elements as specified by code and the output lines generate the corresponding bit combination of code.

A two-level logic diagram may be obtained directly from the Boolean expression derived by maps. There are various other possibilities for a logic diagram that implements this circuit. Now the OR gate whose output is C+D has been used to implement partially each of three outputs.

### Apparatus :

1. XOR gate IC-7486
2. AND gate IC - 7408
3. OR gate IC- 7432
4. NOT gate IC- 7404
5. IC Trainer kit
6. Bread board
7. wires



## LOGIC DIAGRAM :

### 1) Binary to Gray code converter

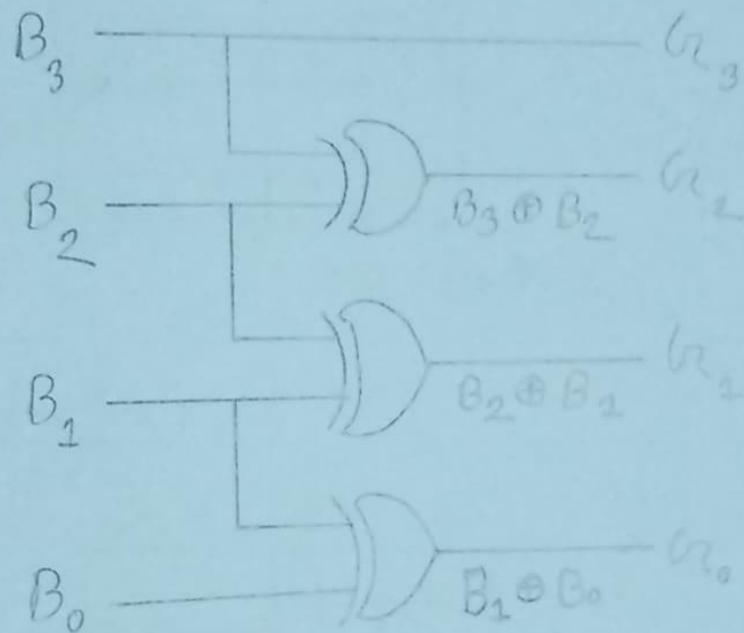


Fig: Logic gate for Binary to Gray

### K-map for $G_3$ :

$B_3 B_2$ \ $B_1 B_0$	00	01	11	10
00				
01				
11	1	1	1	1
10	1	1	1	1

$$G_3 = B_3$$

K-map for  $G_2$ :

$B_1 B_0$ $B_3 B_2$	00	01	11	10
00				
01	1	1	1	1
11				
10	1	1	1	1

$$G_2 = B_3 \oplus B_2$$

K-map for  $G_1$ :

$B_1 B_0$ $B_3 B_2$	00	01	11	10
00			1	1
01	1	1		
11	1	1		
10			1	1

$$G_1 = B_1 \oplus B_2$$

K-map for  $G_0$ :

$B_1 B_0$ $B_3 B_2$	00	01	11	10
00		1		1
01		1		1
11		1		1
10		1		1

$$G_0 = B_1 \oplus B_0$$

### Truth Table:

Binary Input				Binary Code Output			
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

## Logic Diagram:

### Gray code to Binary Converter

$G_3 G_2 G_1 G_0$

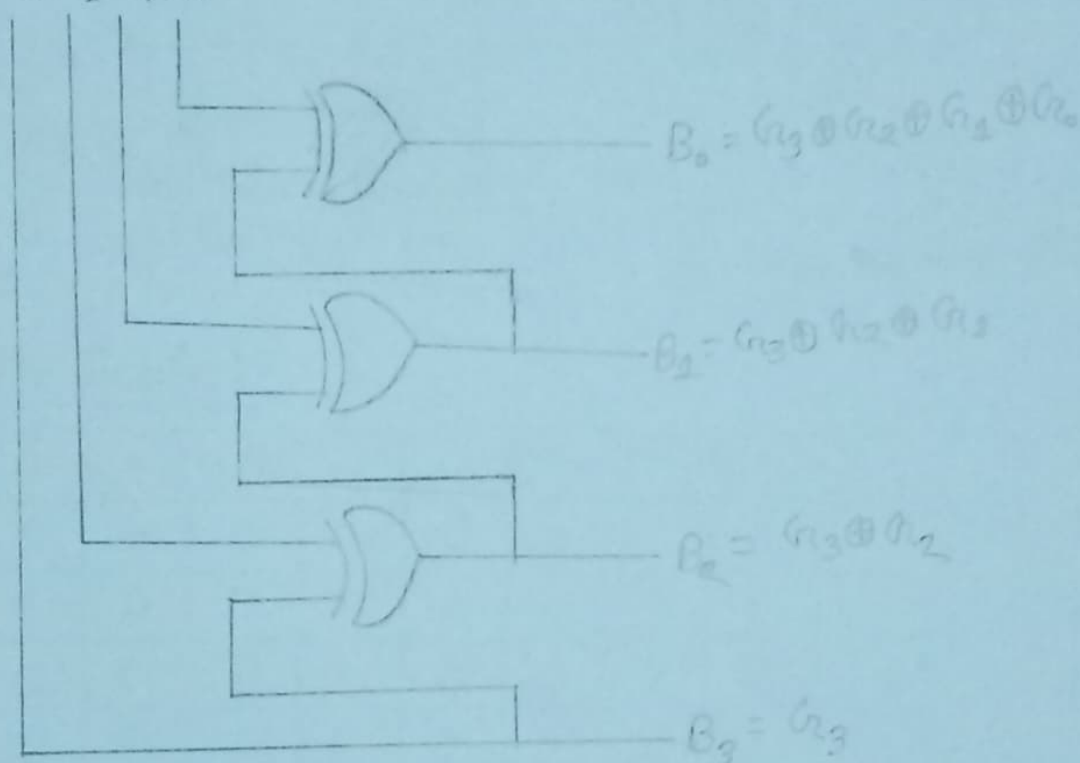


Fig: Gray to binary

#### K-map for $B_3$ :

$G_3 \backslash G_2$	00	01	11	10
00				
01				
11	1	1	1	1
10	1	1	1	1

$$B_3 = G_3$$

#### K map for $B_2$ :

$G_3 \backslash G_2$	00	01	11	10
00				
01	1	1	1	1
11				
10	1	1	1	1

$$B_2 = G_3 \oplus G_2$$



K-Map for B<sub>1</sub>:

$G_3 \backslash G_2$	$G_1 G_0$	00	01	11	10
00				1	1
01		1	1		
11				1	1
10		1	1		

$$B_1 = G_3 \oplus G_2 \oplus G_1$$

Kmap for B<sub>0</sub>:

$G_3 \backslash G_2$	$G_1 G_0$	00	01	11	10
00			1		1
01		1		1	
11			1		1
10		1		1	

$$B_0 = G_3 \oplus G_2 \oplus G_1 \oplus G_0$$

Truth Table:

Gray Code				Binary Code			
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	1	0	0	1	0
0	0	1	0	0	0	1	1
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	1
0	1	0	1	0	1	1	0
0	1	0	0	0	1	1	1
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	1
1	1	1	1	1	0	1	0
1	1	1	0	1	0	1	1
1	0	1	0	1	1	0	0
1	0	1	1	1	1	0	1
1	0	0	1	1	1	1	0
1	0	0	0	1	1	1	1

Logic Diagram:

Binary to Excess-3 Code Converter

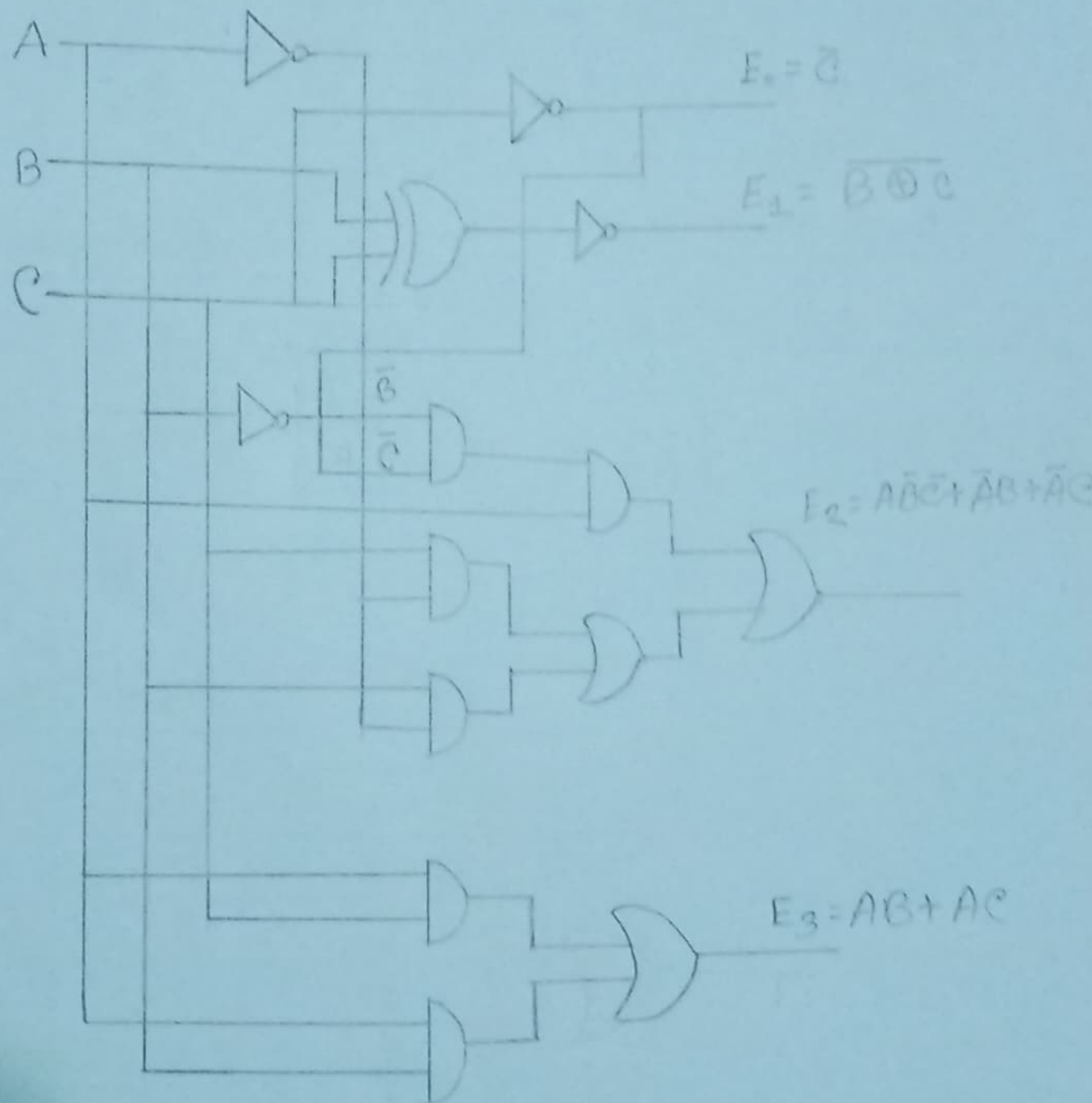


Fig: 3-bit binary to excess+3 Code Converter

K-map for  $E_0$  :

A \ BC	00	01	11	10
0	1			1
1	1			1

$$= \bar{C}$$

K-map for  $E_1$  :

A \ BC	00	01	11	10
0	1		1	
1	1		1	

$$= \bar{B}\bar{C} + B\bar{C} \\ = \bar{B} \oplus \bar{C}$$

K-map for  $E_2$  :

A \ BC	00	01	11	10
0		1	1	1
1	1			

$$= A\bar{B}\bar{C} + \bar{A}B + \bar{A}C$$

K-map for  $E_3$  :

A \ BC	00	01	11	10
0				
1		1	1	1

$$= AB + AC$$

Truth table :

3-bit Binary			Excess-3 Code			
A	B	C	$E_3$	$E_2$	$E_1$	$E_0$
0	0	0	0	0	1	1
0	0	1	0	1	0	0
0	1	0	0	1	0	1
0	1	1	0	1	1	0
1	0	0	0	1	1	1
1	0	1	1	0	0	0
1	1	0	1	0	0	1
1	1	1	1	0	1	0

## Working Procedure:

### 1. Binary to Gray Converter:

- i) Firstly we checked the components and all IC (logic gates) for experiment.
- ii) We separated <sup>binary to Gray</sup> XOR gate (IC 7486) for
- iii) we connected the wires according to the logic circuit.
- iv) Finally, we checked all inputs according to the truth table of binary to Gray.

### 2) Gray to Binary Converter :

- i) Firstly we checked the all components and all IC (logic gates) for experiment.
- ii) We separated XOR gate (IC 7486) for Gray to binary Converter.
- iii) we connected the wires according to the logic circuit.
- iv) Finally, we checked all inputs according to the truth table of Gray to binary Converter.



### 3) 3-bit binary to Excess +3 Code:

- i) Firstly we checked the components and logic gate for examined the binary to Excess +3 code converter.
- ii) We separated XOR gate (IC 7486), NOT gate (IC 7404), AND gate (IC 7408), OR gate (IC 7432).
- iii) We connected the wires according to the binary to excess +3 logic circuit.
- iv) Finally, we checked all inputs according to the truth table of binary to excess +3.

### 4) Excess +3 to binary code converter:

- i) Firstly we checked the components and logic gate for experiment.
- ii) We separated XOR gate, AND gate, OR gate, NOT gate.
- iii) We connected the wires according to the Excess +3 to binary converter.
- iv) Finally, we checked all inputs according to the truth table of Excess +3 code converter.



## Results:

### 1. Binary to Gray converter:

1) we obtained the results using the K-map method —

$$r_3 = B_3, \quad r_2 = B_3 \oplus B_2, \quad r_1 = B_1 \oplus B_2, \quad r_0 = B_1 \oplus B_0$$

### 2) Gray to binary converter:

1) we obtained the results using the K-map method —

$$B_3 = r_3, \quad B_2 = r_3 \oplus r_2, \quad B_1 = r_3 \oplus r_2 \oplus r_1,$$

$$B_0 = r_3 \oplus r_2 \oplus r_1 \oplus r_0$$

### 3) 3-bit binary to Excess + 3 converter:

1) we obtained the results using the K-map method —

$$E_0 = \bar{C}, \quad E_1 = \overline{B \oplus C} \text{ or } E_2 = \overline{B \oplus C} + B \oplus C,$$

$$E_2 = A \bar{B} \bar{C} + \bar{A} C + \bar{A} B, \quad E_3 = A B + A C$$

### Precaution:

- i) Check the connection according to the logic circuit.
- ii) The connection should be properly.
- iii) Check the equipment before starting the experiment.